

2021

ELECTRICAL ENGINEERING

PAPER-I

Time Allowed — 3 Hours

Full Marks — 200

If the questions attempted are in excess of the prescribed number, only the questions attempted first up to the prescribed number shall be valued and the remaining ones ignored.

Answer may be written either in English or in Bengali but all answers must be in one and the same language.

All symbols have their usual significance.

**Group-A**

Answer any three questions.

1. (a) Use superposition theorem to find the value of voltage 'v' in the network of Fig-1. 10



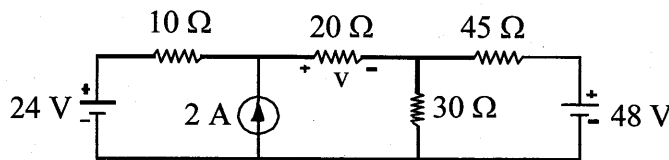


Fig-1

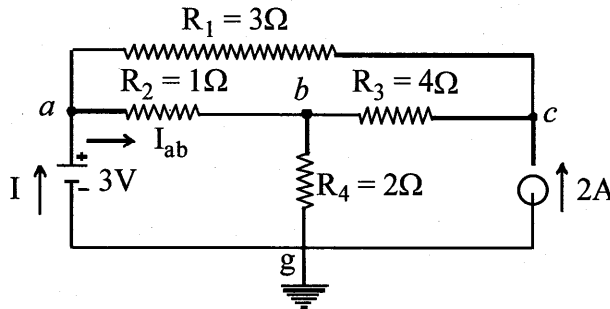
- (b) Find the current through branch 'ab' ( $I_{ab}$ ) and voltage ( $V_{cg}$ ) across the current source using node voltage method. 10



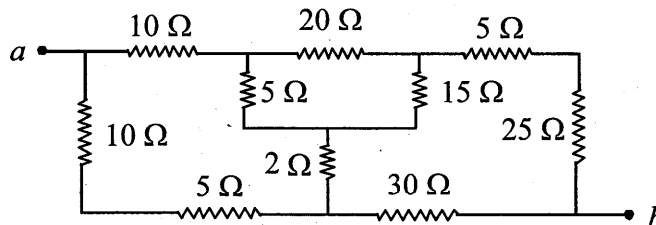
- (c) Determine the resistance between terminals 'ab' of the network shown below. Deduce the formula you have used. 20



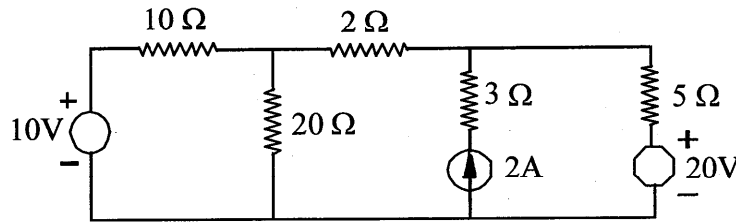
2. (a) Find the voltage across  $2\Omega$  resistor by using superposition theorem for the network shown below. 10



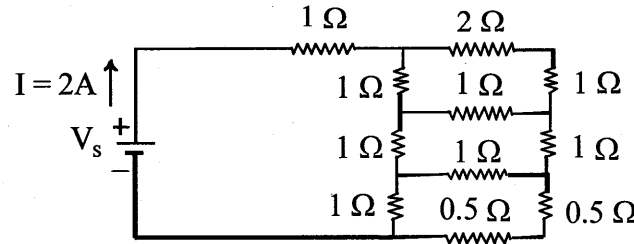
- (b) Find the value of the voltage source ( $V_s$ ) that delivers 2 Amps current the circuit shown below. 10



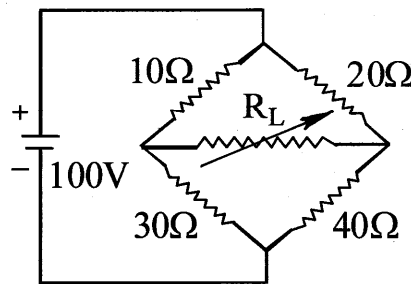- (c) Determine the load resistance  $R_L$ , shown in the circuit below, to receive maximum power from the source; also find the maximum power delivered to the load. 15



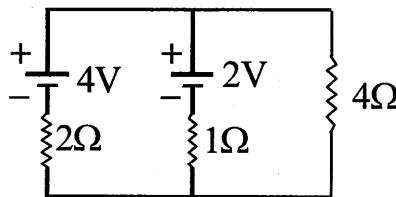
- (d) Using Norton's theorem determine the current flowing through the  $4\Omega$  resistance as shown in the network below. 5




3. (a) A voltage of 120V at 50Hz is applied to a resistance,  $R$  in series with a capacitance  $C$ . The current drawn by the combination is 2A and the power loss in the resistance is 100W. Calculate the values of resistance and capacitance. Draw the phasor diagram. 7+3=10
- (b) A constant voltage of frequency, 1MHz is applied to a lossy inductor in series with a variable capacitor  $C$ . The current drawn is maximum when  $C = 400$  pF; while current is reduced to  $(1/\sqrt{2})$  of the above value, when  $C = 450$  pF. Find the values of resistance and inductance of the inductor. Also calculate the quality factor of the coil and bandwidth of the coil. 10

For guidance of WBCS Prelims , Main Exam and Interview by WBCS Gr A Officers/ Toppers, WBCS Prelims and Main Mock Test (Classroom & Online), Optional Subjects, Studymaterials, Correspondence Course etc. Call WBCSMadeEasy™ at 1800 572 9282 Or 8274048710 Or 9674493673 or mail us at [mailus@wbcsmadeeasy.in](mailto:mailus@wbcsmadeeasy.in)

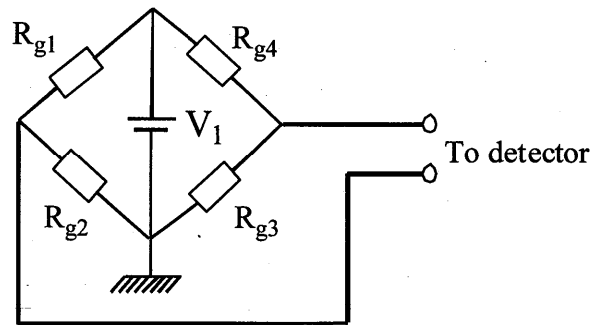- (c) Three loads are delta connected to a symmetrical three phase, 440V system frequency 50Hz. Load A takes 25kW at unity power factor, load B takes 40 kVA at power factor 0.9 leading and load C takes 45 kVA at power factor 0.7 lagging. Calculate the line currents and the readings of two watt meters connected to measure the power input. The current coil of  $W_1$  is connected in line R to the junction of A and C, the current coil of  $W_2$  in line Y to the junction of A and B. Phase sequence RYB. 20
4. (a) Explain the operation of a successive approximation type A/D converter with flowchart. 10
- (b) Find the bridge sensitivity for Wheatstone bridge arrangement based strain measurement system with four identical active strain gauges (i.e. gauge resistances  $R_{g1} = R_{g2} = R_{g3} = R_{g4}$ ) as shown in figure below. 10



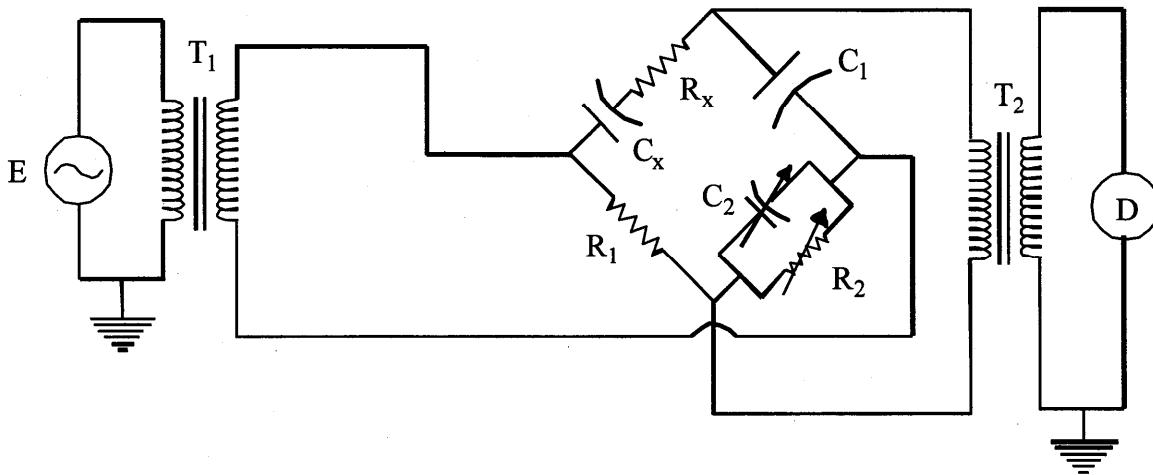- (c) What is the use of Schering bridge? For the following circuit diagram explain bridge balance equation. 10



- (d) Why the CRO probes are to be designed properly for accurate signal representation? Explain with the help of a diagram. 10


For guidance of WBCS Prelims , Main Exam and Interview by WBCS Gr A Officers/ Toppers, WBCS Prelims and Main Mock Test (Classroom & Online), Optional Subjects, Studymaterials, Correspondence Course etc. Call WBCSMadeEasy™ at 1800 572 9282 Or 8274048710 Or 9674493673 or mail us at [mailus@wbcsmadeeasy.in](mailto:mailus@wbcsmadeeasy.in)

5. (a) Determine the minimum value of current gain  $\beta$  required to put the transistor, shown in figure, in saturation when 10


$V_{in} = +5V$

Assume,  $V_{BE(sat)} = 0.8V$ ,

$V_{CE(sat)} = 0.12V$

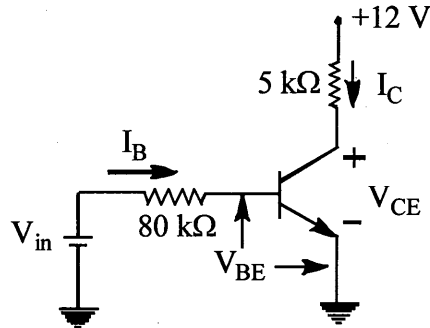

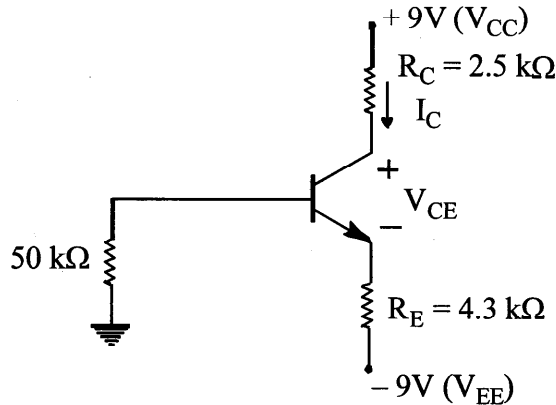- (b) Find the operating point current  $I_{CQ}$  and voltage  $V_{CEQ}$  in the circuit shown below. Given  $V_{BE} = 0.7V$ ,  $\beta$  of transistor is 200. 10



- (c) Simplify the following Boolean function:

$F(A, B, C) = \pi M(0, 1, 5, 7, 8, 9, 15)$

10

- (d) Design all the gates i.e. NOT, AND, OR, NAND, NOR, XOR and XNOR using 2 : 1 multiplexer. 10


**Group-B**

Answer any two questions.


6. (a) Three charges  $q_1, q_2$  and  $q_3$  lie on the  $x$ -axis at  $x = x_1, x_2$  and  $x_3$  respectively. Find the flux produced by all the three charges through a circle of radius  $a$ , normal to the  $x$ -axis with its centre at the origin  $(0, 0, 0)$ . 10

For guidance of WBCS Prelims , Main Exam and Interview by WBCS Gr A Officers/ Toppers, WBCS Prelims and Main Mock Test (Classroom & Online), Optional Subjects, Studymaterials, Correspondence Course etc.Call WBCSMadeEasy™ at 1800 572 9282 Or 8274048710 Or 9674493673 or mail us at [mailus@wbcsmadeeasy.in](mailto:mailus@wbcsmadeeasy.in)

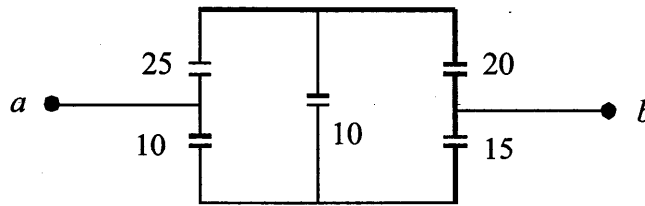- (b) Determine the capacitance of the combination between terminals  $a$  and  $b$  as shown in figure below. All the values of the capacitances are in microfarads. 10




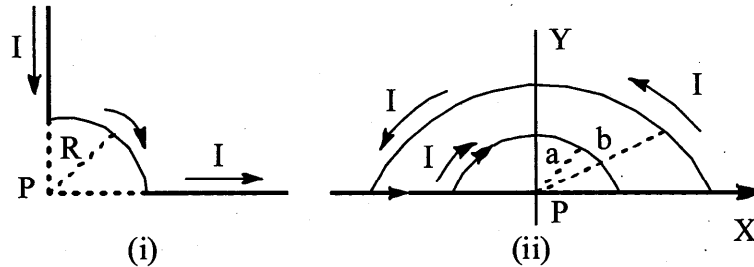- (c) Calculate the magnetic field at point P due to the following current distributions. 10




- (d) Inductance of a closely wound coil is such that when the current changes by 5A per second, it induces electromotive force of 3mv. Furthermore, a steady current of 8A generates in each loop of the coil a magnetic flux of  $40 \mu\text{wb}$ .

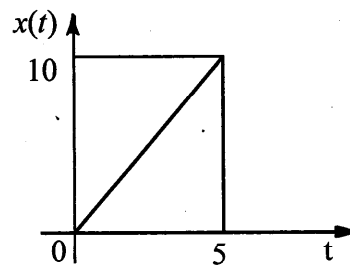- (i) Calculate the inductance of the coil.
  - (ii) Determine the number of loops of the coil. 10
7. (a) Check whether the following signal is a power signal or energy signal 5  
 $x(t) = e^{-\alpha t}, t > 0, \alpha > 0$   
 $= 0, \text{ elsewhere}$
- (b) Resolve  $x(t)$  into even and odd components. 5




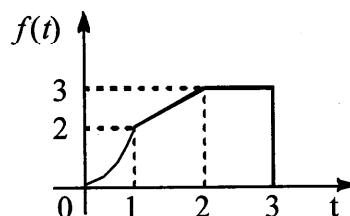- (c) Express following function in terms of singularity functions: 10



For guidance of WBCS Prelims , Main Exam and Interview by WBCS Gr A Officers/ Toppers, WBCS Prelims and Main Mock Test (Classroom & Online), Optional Subjects, Studymaterials, Correspondence Course etc. Call WBCSMadeEasy™ at 1800 572 9282 Or 8274048710 Or 9674493673 or mail us at mailus@wbcsmadeeasy.in

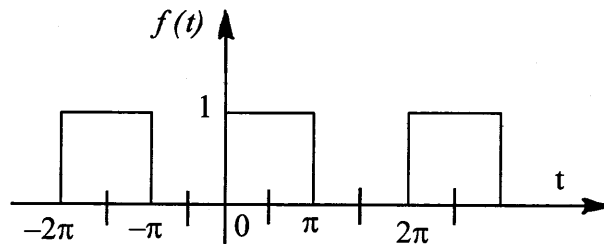(d) Find Fourier coefficients, Amplitude and Phase spectra for the following signal  $f(t)$ . 20



8. (a) A unity feedback system with the following forward path transfer function oscillates at 2 rad/sec.

$$G(s) = \frac{K(s+1)}{s^3 + as^2 + 2s + 1}$$

Find the values of  $K$  and  $a$ .

12

(b) Obtain the transfer function for the system describe by the state-space equations of the form.


$$\dot{x} = Ax + Bu, \quad y = Cx$$

with  $A = \begin{bmatrix} 0 & 1 \\ 0 & -2 \end{bmatrix}$   $B = \begin{bmatrix} 0 \\ 1 \end{bmatrix}$   $C = [1 \quad 0]$

8


(c) Obtain the steady state error for the system shown in figure below, when subjected to a unit step input.

12

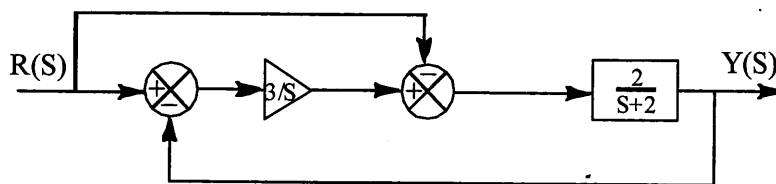


(d) Consider the mechanical system shown in figure below. Obtain the transfer function of the system taking the displacement  $x_i$  as the input and  $x_o$  as the output. Comment whether it is a mechanical load network or lag network.

8

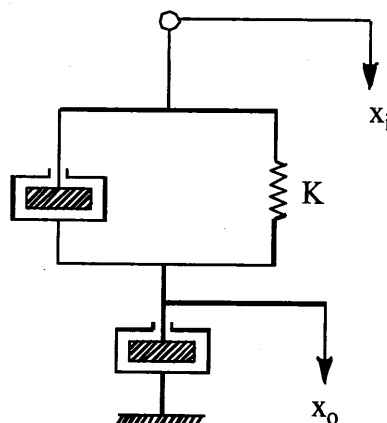


For guidance of WBCS Prelims , Main Exam and Interview by WBCS Gr A Officers/ Toppers, WBCS Prelims and Main Mock Test (Classroom & Online), Optional Subjects, Studymaterials, Correspondence Course etc. Call WBCSMadeEasy™ at 1800 572 9282 Or 8274048710 Or 9674493673 or mail us at [mailus@wbcsmadeeasy.in](mailto:mailus@wbcsmadeeasy.in)

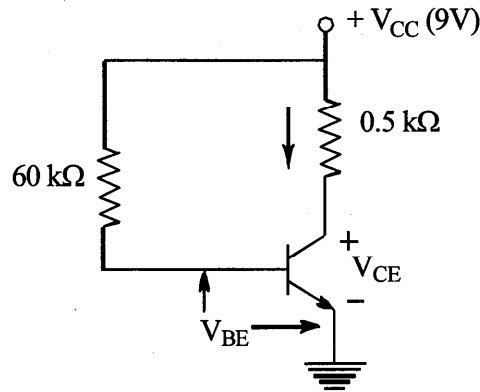
9. (a) The fixed bias circuit shown in figure below is a silicon transistor with  $V_{BE} = 0.7V$ .
- (i) Find the collector current,  $I_C$  and voltage  $V_{CE}$ , if  $\beta$  of transistor is 60.
- (ii) Find  $I_C$  and  $V_{CE}$  if  $\beta$  changes to 80. State what conclusion may be drawn. 15



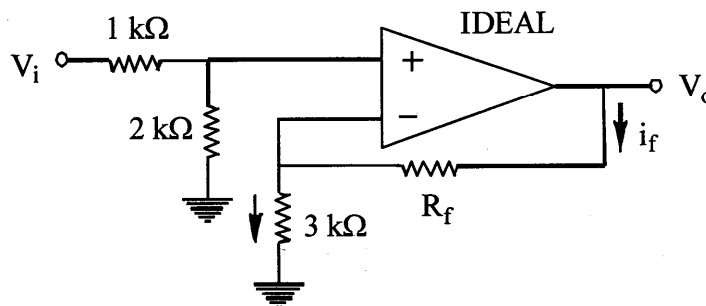- (b) For the ideal op-amp shown, what should be the value of resistor  $R_f$  to obtain a gain of 5? 5



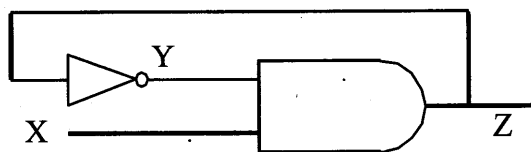- (c) Assume that the inverter in the network below has a propagation delay of 5 ns and the AND gate has a propagation delay of 10 ns. Draw a timing diagram for the network showing X, Y and Z. Assume that X is initially 0, Y is initially 1, X becomes 1 for 80 ns and then X is 0 again. 10



- (d) Write an assembly language program for 8085 microprocessor to multiply two eight bit numbers, the result may contain sixteen bits. 10

For guidance of WBCS Prelims , Main Exam and Interview by WBCS Gr A Officers/ Toppers, WBCS Prelims and Main Mock Test (Classroom & Online), Optional Subjects, Studymaterials, Correspondence Course etc. Call WBCSMadeEasy™ at 1800 572 9282 Or 8274048710 Or 9674493673 or mail us at [mailus@wbcsmadeeasy.in](mailto:mailus@wbcsmadeeasy.in)